 


Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

Question 1


Full adder structure:



Delays:

nmos delays: (3, 4, 5)

pmos delays: (5, 6, 7)

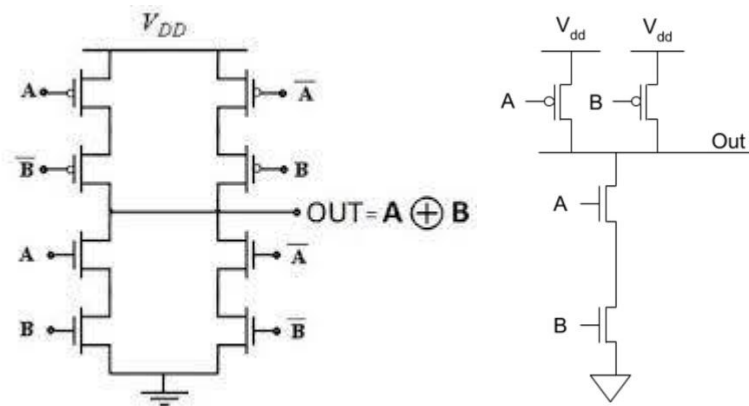

- Inverter gate: (5, 7)
- xor gate: (17, 19) (A=B=0 to B=1, A=1 B=0 to A=0)
- nand gate: (10, 8) (A=B=1 to B=0, A=1 B=0 to B=1)

overall worst case delay:


- Sum: (36, 38) (B=0 A=Cin=1 to A=0, A=Cin=0 B=1 to B=0)
- Cout: (35, 37) (A=B=0 Cin=1 to A=1, A=Cin=1 B=0 to A=0)

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

```
Ln# |  
1 | `timescale 1ns/1ns  
2 |  
3 | module FA(input A, B, Cin, output S, Cout);  
4 |  
5 |     wire y1, y2, y3;  
6 |     xor #(17, 19) g1(y1, A, B), g2(S, y1, Cin);  
7 |     nand #(10, 8) g3(y2, A, B), g4(y3, Cin, y1), g5(Cout, y3, y2);  
8 |  
9 | endmodule  
10 |
```

```
Ln# |  
1 | `timescale 1ns/1ns  
2 |  
3 | module Q1_TB();  
4 |  
5 |     logic a=1, b=0, cin=1;  
6 |     wire cout, s;  
7 |  
8 |     FA full_adder(a, b, cin, s, cout);  
9 |  
10 |  
11 |     initial begin  
12 |         #50 a = 0;  
13 |         #50 cin = 0;  
14 |         #50 b = 1;  
15 |         #50 b = 0;  
16 |         #50 cin = 1;  
17 |         #50 a = 1;  
18 |         #50 a = 0;  
19 |         #50 $stop;  
20 |     end  
21 | endmodule  
22 |
```

 

All the delays are verified using the Verilog code above.

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

Question 2

For calculating the worst case delay of a n-bit ripple-carry adder, we add the worst case delay of n-1 Cout's in addition to the worst case delay of the last Summation (which is longer than the worst case delay of the last Cout). Therefore: delay = (n-1) * 37 + 38


Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module FA_nbit #(parameter n=3) (input [n-1:0] A, B, input Cin, output [n-1:0] S, output Cout);</code>
4	
5	<code> assign #((n-1)*37 + 38) {Cout, S} = A + B + Cin;</code>
6	
7	<code>endmodule</code>
8	

Question 3

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module FA_nbit_TB();</code>
4	
5	<code> logic [3:0] A;</code>
6	<code> logic [3:0] B;</code>
7	<code> logic Cin;</code>
8	<code> wire [3:0] S;</code>
9	<code> wire Cout;</code>
10	<code> parameter n = 4;</code>
11	
12	<code> FA_nbit #(n) fa(A, B, Cin, S, Cout);</code>
13	
14	<code> initial begin</code>
15	
16	<code> repeat(5)</code>
17	<code> begin</code>
18	<code> #160 A = {\$random} % (4'b1111);</code>
19	<code> #160 B = {\$random} % (4'b1111);</code>
20	<code> #160 Cin = {\$random} % (1'b1);</code>
21	<code> end</code>
22	<code> end</code>
23	<code> #160 \$stop;</code>
24	<code>end</code>
25	
26	<code>endmodule</code>
27	

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

 

Question 4

```

Ln#
1  `timescale 1ns/1ns
2
3  module ones_counter_7bit (input [6:0] A, output [2:0] N);
4
5      wire [3:0] in_2bit;
6      parameter n=1;
7      genvar i;
8
9      generate
10         for (i=0; i < 2; i = i + 1) begin: FAs
11             FA_nbit #(n) fa(A[i*3], A[i*3+1], A[i*3+2], in_2bit[i*2], in_2bit[i*2+1]);
12         end
13     endgenerate
14     parameter m = 2;
15     FA_nbit #(m) fa(in_2bit[1:0], in_2bit[3:2], A[6], N[1:0], N[2]);
16
17 endmodule
18

```

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module ones_counter_15bit (input [14:0] A, output [3:0] N);</code>
4	
5	<code> wire [5:0] in_3bit;</code>
6	<code> genvar i;</code>
7	
8	<code> generate</code>
9	<code> for (i=0; i < 2; i = i + 1) begin: onecounters</code>
10	<code> ones_counter_7bit counter(A[i*7+6:i*7], in_3bit[i*3+2:i*3]);</code>
11	<code> end</code>
12	<code>endgenerate</code>
13	
14	
15	<code> parameter m = 3;</code>
16	<code> FA_nbit #(m) fa(in_3bit[2:0], in_3bit[5:3], A[14], N[2:0], N[3]);</code>
17	
18	<code>endmodule</code>
19	

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module ones_counter_31bit (input [30:0] A, output [4:0] N);</code>
4	
5	<code> wire [7:0] in_4bit;</code>
6	<code> genvar i;</code>
7	
8	<code> generate</code>
9	<code> for (i=0; i < 2; i = i + 1) begin: onecounters</code>
10	<code> ones_counter_15bit counter(A[i*15+14:i*15], in_4bit[i*4+3:i*4]);</code>
11	<code> end</code>
12	<code>endgenerate</code>
13	
14	
15	<code> parameter m = 4;</code>
16	<code> FA_nbit #(m) fa(in_4bit[3:0], in_4bit[7:4], A[30], N[3:0], N[4]);</code>
17	
18	<code>endmodule</code>
19	

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module ones_counter_63bit (input [62:0] A, output [5:0] N);</code>
4	
5	<code> wire [9:0] in_5bit;</code>
6	<code> genvar i;</code>
7	
8	<code> generate</code>
9	<code> for (i=0; i < 2; i = i + 1) begin: onecounters</code>
10	<code> ones_counter_31bit counter(A[i*31+30:i*31], in_5bit[i*5+4:i*5]);</code>
11	<code> end</code>
12	<code>endgenerate</code>
13	
14	
15	<code> parameter m = 5;</code>
16	<code> FA_nbit #(m) fa(in_5bit[4:0], in_5bit[9:5], A[62], N[4:0], N[5]);</code>
17	
18	<code>endmodule</code>
19	

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

```
Ln# |  
1 | `timescale 1ns/1ns  
2 |  
3 | module ones_counter_127bit (input [126:0] A, output [6:0] N);  
4 |  
5 |     wire [11:0] in_6bit;  
6 |     genvar i;  
7 |  
8 |     generate  
9 |     for (i=0; i < 2; i = i + 1) begin: onecounters  
10 |         ones_counter_63bit counter(A[i*63+62:i*63], in_6bit[i*6+5:i*6]);  
11 |     end  
12 | endgenerate  
13 |  
14 |  
15 |     parameter m = 6;  
16 |     FA_nbit #(m) fa(in_6bit[5:0], in_6bit[11:6], A[126], N[5:0], N[6]);  
17 |  
18 | endmodule  
19 |
```

Question 5


Test bench that produces 127-bit marching-1 data that covers all the bits:

```
Ln# |  
1 | `timescale 1ns/1ns  
2 | module counter_127bit_TB ();  
3 |  
4 |     logic [126:0] A = 1'd0;  
5 |     wire [6:0] N;  
6 |  
7 |     ones_counter_127bit counter(A, N);  
8 |  
9 |     initial begin  
10 |         repeat(127)  
11 |         begin  
12 |             #1000 A = 2*A + 1;  
13 |         end  
14 |         repeat(127)  
15 |         begin  
16 |             #1000 A = A*2;  
17 |         end  
18 |         #1000 $stop;  
19 |     end  
20 |  
21 | endmodule  
22 |
```

Picture of the waveform:


Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

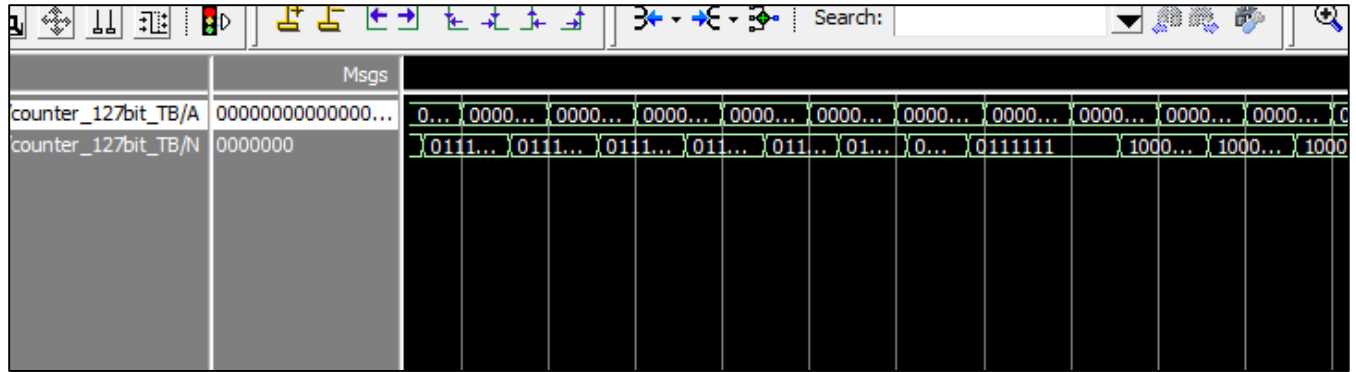


Waveform produced by this bench is too large to prove anything on a screenshot. Therefore, instead of that, this bench is used:

```
Ln#  
1  `timescale 1ns/1ns  
2  module counter_127bit_TB_final ();  
3  
4      logic [126:0] A = 1'd0;  
5      wire [6:0] N;  
6  
7      ones_counter_127bit counter(A, N);  
8      initial begin  
9          repeat(8)  
10             begin  
11                 #1000 A = 2*A + 1;  
12             end  
13         repeat(10)  
14             begin  
15                 #1000 A = A*2;  
16             end  
17         repeat(5)  
18             begin  
19                 #1000 A = {$random} % (1'd1);  
20             end  
21         #1000 $stop;  
22     end  
23  
24 endmodule
```

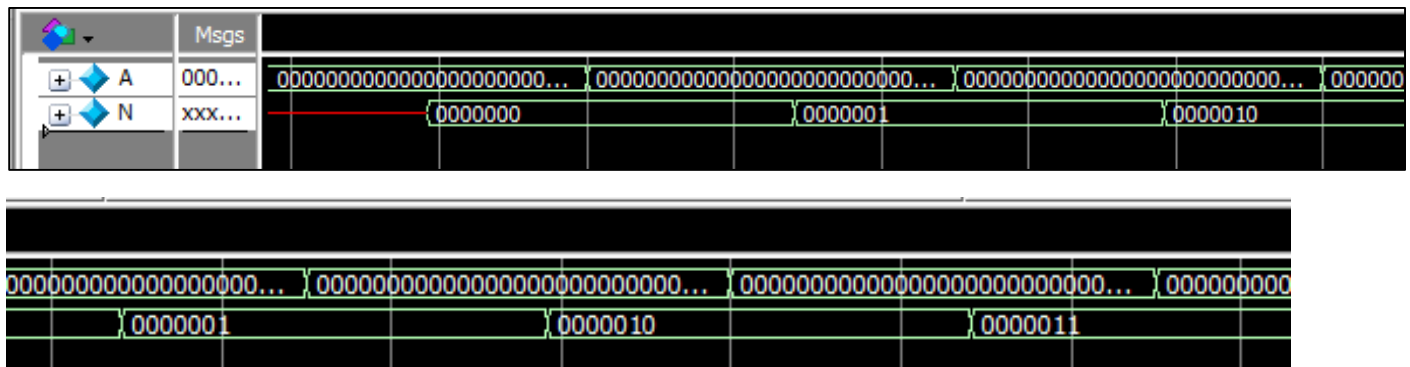

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

 

Again only some parts of the waveform are shown, due to its length.

Question 6

Delay of the one's counter of part 4:

$$38 * 6 + 37 * (0+1+2+3+4+5) = 783 = 19783 - 19000$$



```

Ln#
1  `timescale 1ns/1ns
2
3  module ones_counter_127bit_Q6 (input [126:0] A, output reg [6:0] N);
4      integer i;
5      always @(A) begin
6          #783 N = 7'b0000000;
7          for (i=0; i<127; i=i+1) begin
8              if (A[i]==1'b1)
9                  N=N+(1'b1);
10             end
11         end
12     endmodule
13

```


Samira Hajizadeh - 810198378

The screenshot displays a logic analyzer interface with two channels. The top channel, labeled `/counter_12bit_Q...`, shows a hexadecimal value of `0000000000000000` and a binary value of `0111111011111111`. The bottom channel, also labeled `/counter_12bit_Q...`, shows a hexadecimal value of `00000000` and a binary value of `0111111011111111`. The time scale at the bottom ranges from `193500 ns` to `196500 ns`. The interface includes a status bar at the bottom with the text "Now 255000 ns" and "Cursor 1 0 ns".

Question 7

Q4's one's counter:

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

```
=== design hierarchy ===  
  
ones_counter_127bit      1  
  $paramod\FA_nbit\n=6   1  
    ones_counter_63bit   2  
      $paramod\FA_nbit\n=5 1  
        ones_counter_31bit 2  
          $paramod\FA_nbit\n=4 1  
            ones_counter_15bit 2  
              $paramod\FA_nbit\n=3 1  
                ones_counter_7bit 2  
                  $paramod\FA_nbit\n=1 2  
                    $paramod\FA_nbit\n=2 1  
  
Number of wires:      777  
Number of wire bits:  1759  
Number of public wires: 408  
Number of public wire bits: 1390  
Number of memories:   0  
Number of memory bits: 0  
Number of processes:  0  
Number of cells:      552  
  $_AND_               46  
  $_AOI3_              46  
  $_NAND_              83  
  $_NOR_               3  
  $_NOT_               46  
  $_OAI3_              82  
  $_OR_                6  
  $_XNOR_              128  
  $_XOR_               112
```

```
4.6.2. Re-integrating ABC results.  
ABC RESULTS:      NAND cells:      18  
ABC RESULTS:      NOR cells:       39  
ABC RESULTS:      NOT cells:       19  
ABC RESULTS:      internal signals: 25  
ABC RESULTS:      input signals:   13  
ABC RESULTS:      output signals:   7  
Removing temp directory.
```

Q6's one's counter:

Digital Systems 1 – Computer Assignment 3

Samira Hajizadeh - 810198378

```
=== ones_counter_127bit_Q6 ===  
  
Number of wires:          3189  
Number of wire bits:      3321  
Number of public wires:   2  
Number of public wire bits: 134  
Number of memories:       0  
Number of memory bits:    0  
Number of processes:      0  
Number of cells:          3194  
  $ _AND_                  244  
  $ _AOI3_                 592  
  $ _MUX_                  496  
  $ _NAND_                 134  
  $ _NOR_                  837  
  $ _NOT_                  13  
  $ _OAI3_                 9  
  $ _OR_                   9  
  $ _XNOR_                 620  
  $ _XOR_                  240  
  
2.24. Executing CHECK pass (checking for obvious problems).  
checking module ones_counter_127bit_Q6..  
found and reported 0 problems.
```

```
4.1.2. Re-integrating ABC results.  
ABC RESULTS:          NAND cells:      1314  
ABC RESULTS:          NOR cells:       1795  
ABC RESULTS:          NOT cells:       536  
ABC RESULTS:          internal signals: 3187  
ABC RESULTS:          input signals:   127  
ABC RESULTS:          output signals:   7  
Removing temp directory.
```

The result of the second module uses way more gates and leads to a higher power consumption due to the fact that the yosys's path is not always the optimized one. In the first case, because we elaborated the design for yosys the result uses ten times less gates.