
 


Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

Question 1

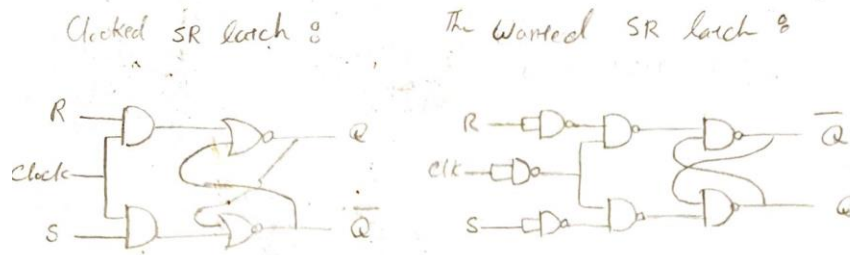

Delays:

- Nmos: 4
- Pmos: 6
- Nand: 8
- SR latch: 32 (4 times of nand gate)


```
Ln# |  
1   | `timescale 1ns/1ns  
2   |  
3   | module SR_latch(input S, R, Clk, output Q);  
4   |  
5   |     wire Rbar, Clkbar, Sbar, y1, y2, Qbar;  
6   |  
7   |  
8   |     nand #8 g1(Rbar, R, R), g2(Clkbar, Clk, Clk), g3(Sbar, S, S);  
9   |     nand #8 g4(y1, Rbar, Clkbar), g5(y2, Sbar, Clkbar);  
10  |     nand #8 g6(Q, Qbar, y2), g7(Qbar, Q, y1);  
11  |  
12  |  
13  | endmodule  
14  |
```

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

 Question 2

```
Ln#
1  `timescale 1ns/1ns
2
3  module SR_latch_TB();
4
5      logic s=0, r=1, c=0;
6      wire q;
7
8      SR_latch l(s, r, c, q);
9
10     initial begin
11         #40 c=1;
12         #40 s=1; r=0;
13         #40 c=0;
14         #40 c=1;
15         #40 s=0; r=0;
16         #40 c=0;
17         #40 c=1;
18         #40 s=0; r=1;
19         #40 c=0;
20         #40 c=1;
21         #40 s=0; r=0;
22         #40 c=0;
23         #40 $stop;
24     end
25
26 endmodule
27
```




- First two rectangles: After turning on the active low input clock, the output drops to zero as a result of being reset. In the second rectangle we see after assigning 0 to S and R, and enabling the clock the output has changed to 1.
- Second two rectangles: In here the process of giving 0 value to S and R has been repeated but this time the output remains the same

From the two above conditions we understand that giving 0 value to both R and S simultaneously results in memory loss.

Digital Systems 1 – Computer Assignment 4
Samira Hajizadeh - 810198378


Question 3

 

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	
3	<code>module D_latch(input D, Clk, output Q);</code>
4	<code> wire dbar;</code>
5	<code> not (dbar, D);</code>
6	<code> SR_latch l(D, dbar, Clk, Q);</code>
7	
8	
9	<code>endmodule</code>
10	
11	
12	<code>module D_latch_TB();</code>
13	
14	<code> logic d=0;</code>
15	<code> logic c=0;</code>
16	<code> wire q;</code>
17	<code> D_latch l(d, c, q);</code>
18	
19	<code> initial begin</code>
20	<code> #40 d=1;</code>
21	<code> #40 c=1;</code>
22	<code> #40 d=0;</code>
23	<code> #40 c=0;</code>
24	<code> #40 d=1;</code>
25	<code> #40 \$stop;</code>
26	<code> end</code>
27	
28	<code>endmodule</code>


Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

 

As shown in the above picture, the circuit works as expected.

Question 4

 


Question 5

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

```
Ln#
1  `timescale 1ns/1ns
2
3  module ShiftRegister8bit(input SID, Clk, output [7:0] Q);
4
5      wire [7:0] y;
6      assign y[7] = SID;
7      genvar i;
8      generate
9      for (i=7; i >= 0; i=i-1) begin
10          D_latch l(y[i], Clk, Q[i]);
11          if (i > 0) assign y[i-1] = Q[i];
12      end
13      endgenerate
14
15  endmodule
16
17  module SR_8bit_TB();
18
19      logic s=0, c=0;
20      wire [7:0] q;
21
22      ShiftRegister8bit SR(s, c, q);
23
24      initial begin
25          #300 s=1;
26          #300 s=0;
27          #300 c=1;
28          #300 s=1;
29          #300 c=0;
30          #300 $stop;
31      end
32
33  endmodule
```


Waveform:

 

Digital Systems 1 – Computer Assignment 4


Samira Hajizadeh - 810198378

A part of the waveform:

 

Explanation: There is no barrier between each input and the one next to it therefore the SID effects all bits simultaneously.

Question 6

 

```

Ln#
1  `timescale 1ns/1ns
2
3  module D_mmff(input D, Clk, output Q);
4
5      wire y;
6      D_latch l1(D, Clk, y), l2(y, ~Clk, Q);
7
8  endmodule
9

```

Question 7

```

Ln#
1  `timescale 1ns/1ns
2
3  module D_mmff_rs(input D, RS, Clk, output Q);
4
5      D_mmff d(D|RS, Clk, Q);
6  endmodule

```

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378


Question 8

```

Ln#
1  `timescale 1ns/1ns
2
3  module ShiftRegister8bit_2(input SID, RS, Clk, output [7:0] Q);
4
5      wire [7:0] y;
6      assign y[7] = SID;
7      genvar i;
8      generate
9      for (i=7; i >= 0; i=i-1) begin
10          D_mmff_rsl(y[i], RS, Clk, Q[i]);
11          if (i > 0) assign y[i-1] = Q[i];
12      end
13      endgenerate
14
15  endmodule
16
17  module SR_8bit_2_TB();
18
19      logic s=1, c=1, r=0;
20      wire [7:0] q;
21
22      ShiftRegister8bit_2 SR(s, r, c, q);
23
24      initial begin
25          repeat (16) #600 c=~c;
26          #600 r=1;
27          repeat (2) #600 c=~c;
28          #600 r=0;
29          repeat (2) #600 c=~c;
30          #600 s=1;
31          repeat (16) #600 c=~c;
32          #600 r=1;
33          repeat (2) #600 c=~c;
34          #600 $stop;
35      end
36
37  endmodule


```

Waveform:

 

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

 

Explanation: In spite of the circuit of problem 4, this shift register has the ability to be initially set to zero. In problem 4, this initialization was not approachable and as a result the shifter did not work well.

Question 9


```
Ln#
1  `timescale 1ns/1ns
2
3  module ShiftRegister8bit_3(input SID, RS, Clk, output logic [7:0] Q);
4
5      always @(posedge Clk) begin
6          if (RS) assign Q = 7'b0;
7          else begin
8              assign Q = {SID, Q[7:1]};
9          end
10     end
11
12 endmodule
13
14 module SR_8bit_3_TB();
15
16     logic s=1, c=1, r=0;
17     wire [7:0] q;
18
19     ShiftRegister8bit_3 SR(s, r, c, q);
20
21     initial begin
22         repeat (16) #600 c=~c;
23         #600 r=1;
24         repeat (2) #600 c=~c;
25         #600 r=0;
26         repeat (2) #600 c=~c;
27         #600 s=1;
28         repeat (16) #600 c=~c;
29         #600 r=1;
30         repeat (2) #600 c=~c;
31         #600 $stop;
32     end
33
34 endmodule
35
```

Waveform:

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

Waveform:

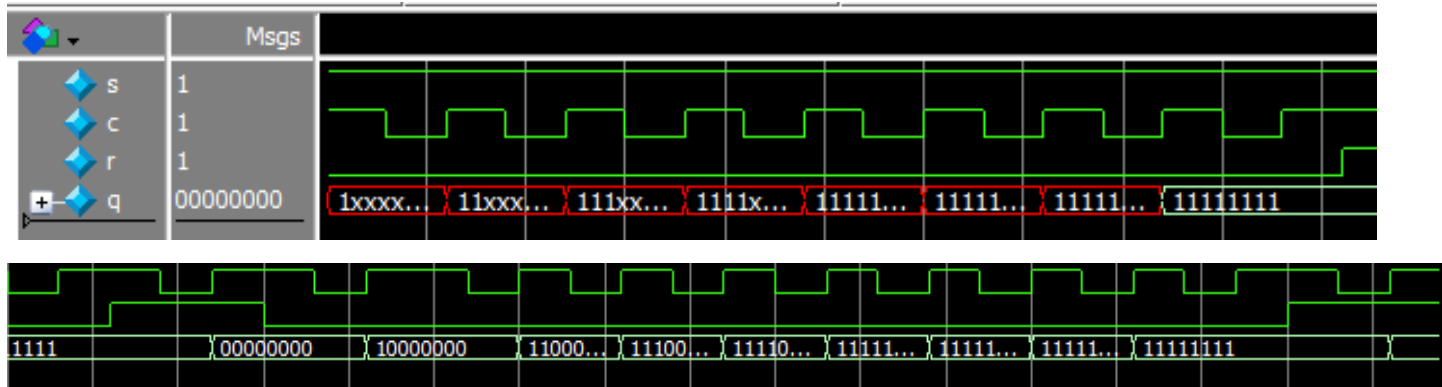

As seen above, the waveform is totally equal to the one of question 8.

Question 10

```


Ln#
1      `timescale 1ns/1ns
2
3      module LFSR(input RS, Clk, output logic [7:0] Q);
4
5          ShiftRegister8bit_3 sr(SID, RS, Clk, Q);
6          assign SID = Q[7]^Q[6]^Q[3]^Q[0];
7
8      endmodule
9
10     module LFSR_TB();
11
12         logic c=1, r=0;
13         wire [7:0] q;
14
15         LFSR SR(r, c, q);
16
17         initial begin
18
19             repeat (2) #600 c=~c;
20             #600 r=1;
21             repeat (2) #600 c=~c;
22             #600 r=0;
23
24             repeat (40) #600 c=~c;
25             #600 $stop;
26         end
27
28     endmodule
29

```

Digital Systems 1 – Computer Assignment 4


Samira Hajizadeh - 810198378

 With the assumptions of the question, the output is always equal to zero.



The corrected circuit






```
Ln#
1  `timescale 1ns/1ns
2
3  module LFSR(input SID, RS, Clk, output logic [7:0] Q);
4      xor g(SID, Q[7], Q[6], Q[5], Q[1], Q[0], 1'b1);
5      ShiftRegister8bit_3 sr(SID, RS, Clk, Q);
6
7  endmodule
8
9  module LFSR_TB();
10
11      logic c=1, r=1;
12      wire s;
13      wire [7:0] q;
14
15      LFSR SR(s, r, c, q);
16
17      initial begin
18          #600 r=1; c=1;
19          repeat (2) #600 c=~c;
20          #600 r=0;
21          repeat (50) #600 c=~c;
22          #600 $stop;
23      end
24
25  endmodule
26
```

 

Digital Systems 1 – Computer Assignment 4


Samira Hajizadeh - 810198378

00000000 -> 01000000 -> 00100000 -> 01000100 -> 10010001 -> 11001000 -> 01110010 -> 10100111
 11010011 -> 11101001 -> 01111010 -> 10011110 -> 11001111 -> 01011100 -> 01011100 -> 01001011 ->
 10010010 -> 10101100 -> 10101011 -> 01101010 -> 10011010 -> 01100110 -> 00110011 -> 00011001 ->
 >10000110 -> 11000011 -> 11100001 -> 10111100 -> 10101111 -> 11011011 -> 11101101 ->
 11110110 -> 01111101 -> 01001111 -> 00100111 -> 10001001 -> 11000100

     

Digital Systems 1 – Computer Assignment 4

Samira Hajizadeh - 810198378

 

The period of this circuit is long enough to be used as a random code producer with a particular seed.