 


Question 1

A)



B) As indicated in the last computer assignment, the calculated to 0 and to 1 delays are 28 and 32 respectively.

C)

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	<code>module MUX4to1(a, b, c, d, s0, s1, w);</code>
3	
4	<code>input a, b, c, d, s0, s1;</code>
5	<code>output w;</code>
6	
7	<code>assign #(32,28) w = s1 ? (s0 ? d : c) : (s0 ? b : a);</code>
8	
9	<code>endmodule</code>
10	<code> </code>


Digital Systems 1 – CA2
Samira Hajizadeh 810198378

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	<code>module TB();</code>
3	<code> logic aa=1, bb=1, cc=1, dd=0, ss0=0, ss1=0;</code>
4	<code> wire ww;</code>
5	<code> MUX4to1 mux(aa, bb, cc, dd, ss0, ss1, ww);</code>
6	<code> initial begin</code>
7	<code> #1080 cc=0;</code>
8	<code> #80 dd=1;</code>
9	<code> #80 aa=0;</code>
10	<code> #80 bb=0;</code>
11	<code> #80 ss0=1;</code>
12	<code> #80 aa=1;</code>
13	<code> #80 cc=1;</code>
14	<code> #80 aa=1;</code>
15	<code> #80 ss0=0;</code>
16	<code> #80 dd=0;</code>
17	<code> #80 aa=0;</code>
18	<code> #80 bb=1;</code>
19	
20	<code> #80 \$stop;</code>
21	<code> end</code>
22	
23	<code>endmodule</code>

D)


Name	Status	Type	Order
BS_16bit_TB.sv	✓	SystemVerilog 7	
BS_16bit.sv	✓	SystemVerilog 6	
BS_4bit_TB.sv	✓	SystemVerilog 3	
16to1MUX_TB.sv	✓	SystemVerilog 5	
16to1MUX.sv	✓	SystemVerilog 4	
4to1MUX_TB.sv	✓	SystemVerilog 2	
4to1MUX.sv	✓	SystemVerilog 0	
4bitBarrelShifter.s...	✓	SystemVerilog 1	

E)

 

Question 2

A)

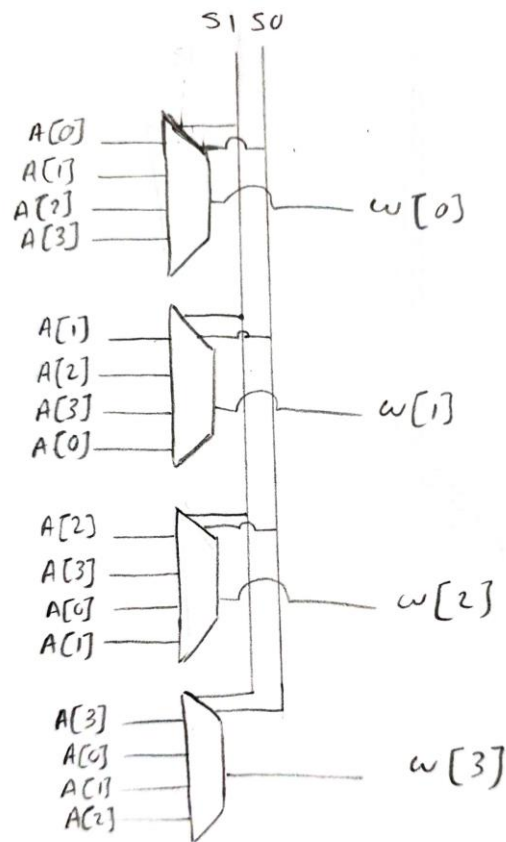

B) multiplexers delays are: (32, 28)

Four multiplexers produce the results. If all of A array's members are not the same and s0 and s1 are not equal to 0, then there will be a to 0 change in at least one of the multiplexers.

Worst case delay: 32

C)

Ln#	
1	<code>`timescale 1ns/1ns</code>
2	<code>module BS_4bit(input [1:0] s, [3:0] A, output [3:0] w);</code>
3	
4	<code> MUX4to1 mux1(A[0], A[1], A[2], A[3], s[0], s[1], w[0]),</code>
5	<code> mux2(A[1], A[2], A[3], A[0], s[0], s[1], w[1]),</code>
6	<code> mux3(A[2], A[3], A[0], A[1], s[0], s[1], w[2]),</code>
7	<code> mux4(A[3], A[0], A[1], A[2], s[0], s[1], w[3]);</code>
8	
9	<code>endmodule</code>
10	<code> </code>

Digital Systems 1 – CA2
Samira Hajizadeh 810198378

D)


```

Ln#
1  `timescale 1ns/1ns
2  module BS_4bit_TB();
3      logic [3:0]A=0111;
4      logic [1:0]s=00;
5      wire [3:0] w;
6
7      BS_4bit BS4bit(s , A , w);
8
9      initial begin
10         #80 s[0]=1;
11         #80 A[3]=1;
12         #80 A[0]=0;
13         #80 s[0]=1;
14         #80 A[1]=0;
15         #80 A[2]=1;
16         #80 s[1]=1;
17         #80 A[0]=1;
18         #80 s[0]=0;
19
20         #80 $stop;
21     end
22
23 endmodule

```


Name	Status	Type	Order
BS_16bit_TB.sv	✓	SystemVerilog	7
BS_16bit.sv	✓	SystemVerilog	6
BS_4bit_TB.sv	✓	SystemVerilog	3
16to1MUX_TB.sv	✓	SystemVerilog	5
16to1MUX.sv	✓	SystemVerilog	4
4to1MUX_TB.sv	✓	SystemVerilog	2
4to1MUX.sv	✓	SystemVerilog	0
4bitBarrelShifter.s...	✓	SystemVerilog	1

E)

 

Question 3

A)

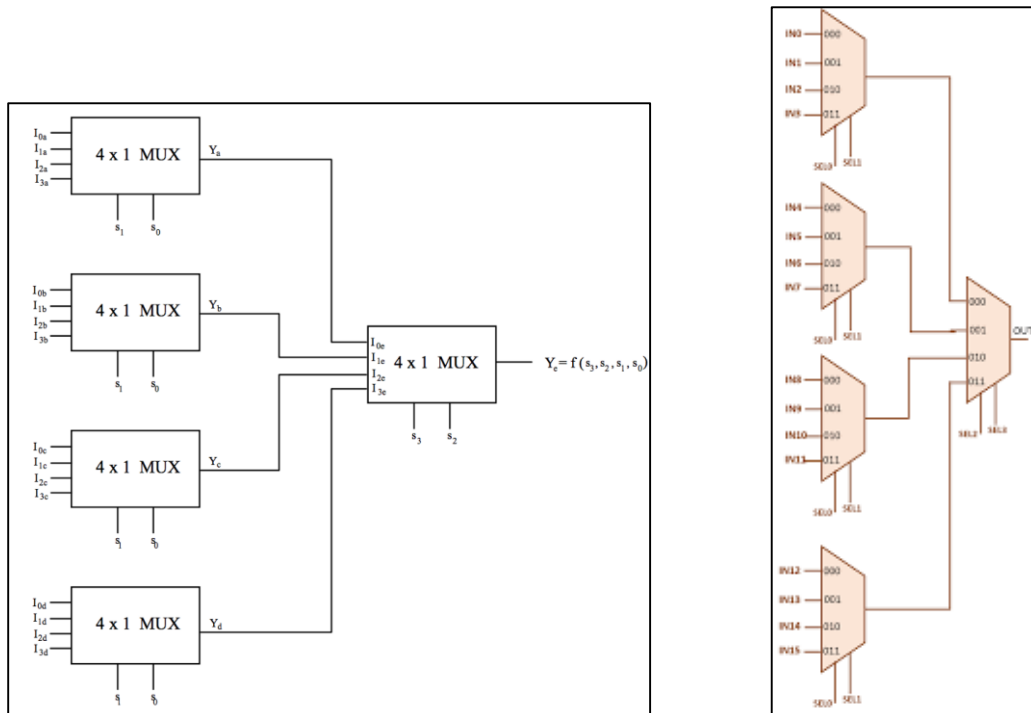

B) multiplexers delays are: (32, 28)

If s₀=s₁=s₂=s₃=1, then the output is set to the fifteenth output. By changing in₁₅ from 0 to 1 the total delay will be 2 to 1 delays: 2 * 32 = 64

By going from s₀=s₁=s₂=s₃=in₁₅=1 to in₁₅=0 we will have two to 0 delays: 2 * 28 = 56

Worst case delay: To 0 = 64, To 1 = 56

C)

```

Ln#
1  `timescale 1ns/1ns
2  module MUX16to1(A, s, w);
3
4      input [15:0] A;
5      input [3:0] s;
6      output w;
7      wire y1, y2, y3, y4;
8
9      MUX4to1 mux1(A[0], A[1], A[2], A[3], s[0], s[1], y1),
10     mux2(A[4], A[5], A[6], A[7], s[0], s[1], y2),
11     mux3(A[8], A[9], A[10], A[11], s[0], s[1], y3),
12     mux4(A[12], A[13], A[14], A[15], s[0], s[1], y4),
13     mux5(y1, y2, y3, y4, s[2], s[3], w);
14
15  endmodule

```

Digital Systems 1 – CA2
Samira Hajizadeh 810198378

```


Ln#
1  `timescale 1ns/1ns
2  module TB_16to1MUX();
3
4      logic [15:0]A= 'b0111111111111111;
5      logic [3:0]s=1111;
6      wire w;
7
8      MUX16to1 mux(A, s, w);
9
10     initial begin
11         #80 A[15]=1;
12         #80 A[7]=0;
13         #80 s[0]=0;
14         #80 A[7]=1;
15         #80 A[3]=0;
16         #80 s[0]=1;
17         #80 s[1]=0;
18
19         #80 $stop;
20     end
21
22 endmodule
23

```

D)


Name	Status	Type	Ord
BS_16bit_TB.sv	✓	SystemVerilog 7	
BS_16bit.sv	✓	SystemVerilog 6	
BS_4bit_TB.sv	✓	SystemVerilog 3	
16to1MUX_TB.sv	✓	SystemVerilog 5	
16to1MUX.sv	✓	SystemVerilog 4	
4to1MUX_TB.sv	✓	SystemVerilog 2	
4to1MUX.sv	✓	SystemVerilog 0	
4bitBarrelShifter.s...	✓	SystemVerilog 1	

E)

 

Question 4

A)

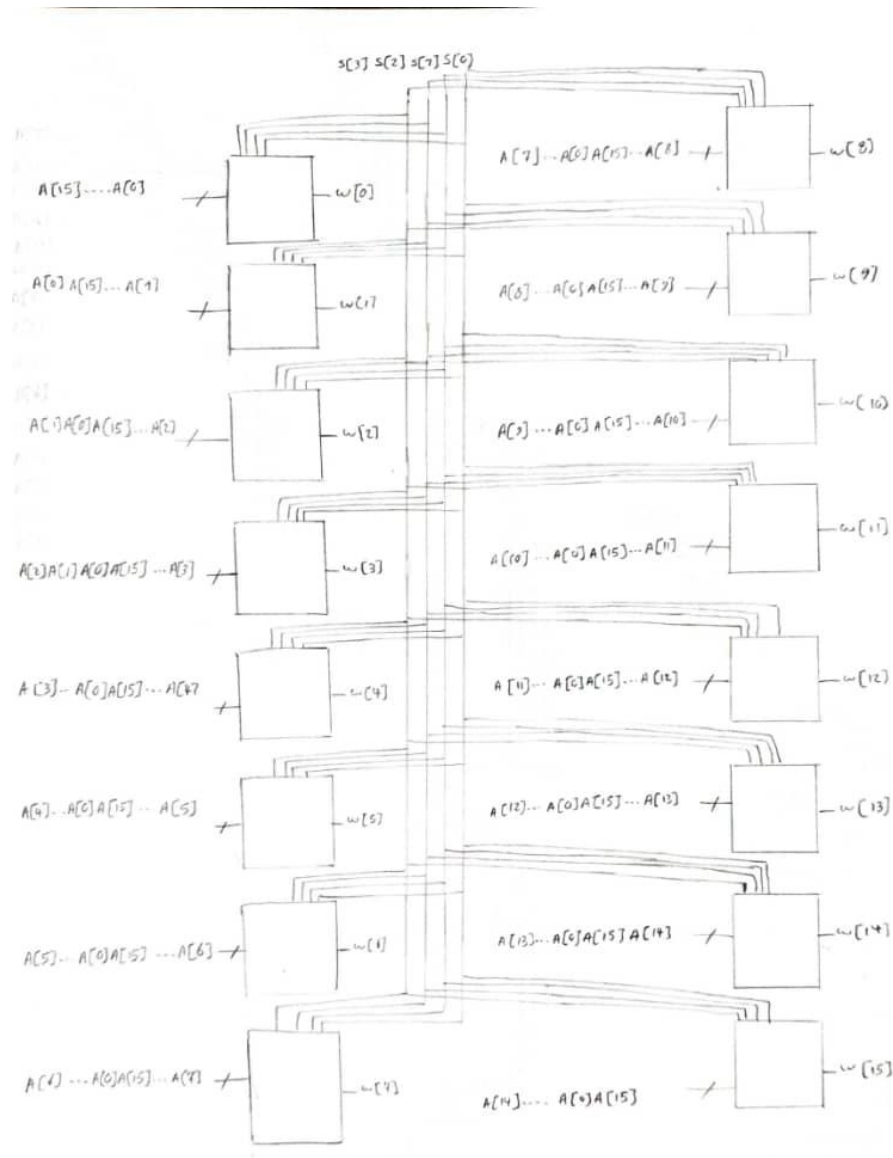

B)

16 16-to-1 multiplexers operate simultaneously, therefore the worst case delay is equal to to-1 delay of multiplexer: 64

C)

Digital Systems 1 – CA2
Samira Hajizadeh 810198378

```

Ln#
1  `timescale 1ns/1ns
2  module BS_16bit(input [15:0] A, [3:0] s, output [15:0] w);
3
4      MUX16to1 mux1(A[15:0], s, w[0]),
5          mux2({A[0], A[15:1]}, s, w[1]),
6          mux3({A[1:0], A[15:2]}, s, w[2]),
7          mux4({A[2:0], A[15:3]}, s, w[3]),
8          mux5({A[3:0], A[15:4]}, s, w[4]),
9          mux6({A[4:0], A[15:5]}, s, w[5]),
10         mux7({A[5:0], A[15:6]}, s, w[6]),
11         mux8({A[6:0], A[15:7]}, s, w[7]),
12         mux9({A[7:0], A[15:8]}, s, w[8]),
13         mux10({A[8:0], A[15:9]}, s, w[9]),
14         mux11({A[9:0], A[15:10]}, s, w[10]),
15         mux12({A[10:0], A[15:11]}, s, w[11]),
16         mux13({A[11:0], A[15:12]}, s, w[12]),
17         mux14({A[12:0], A[15:13]}, s, w[13]),
18         mux15({A[13:0], A[15:14]}, s, w[14]),
19         mux16({A[14:0], A[15]}, s, w[15]);
20
21  endmodule
22

```

```

Ln#
1  `timescale 1ns/1ns
2  module BS_16bit_TB();
3
4      logic [15:0]A= 'b1111111111111110;
5      logic [3:0]s=1111;
6      wire [15:0]w;
7
8      BS_16bit bs(A, s, w);
9
10     initial begin
11         #80 A[0]=1;
12         #80 A[7]=0;
13         #80 s[0]=0;
14         #80 A[7]=1;
15         #80 A[3]=0;
16         #80 s[0]=1;
17         #80 s[1]=0;
18
19         #80 $stop;
20     end
21
22  endmodule
23

```

D)

Name	Status	Type	Or
BS_16bit_TB.sv	✓	SystemVerilog 7	
BS_16bit.sv	✓	SystemVerilog 6	
BS_4bit_TB.sv	✓	SystemVerilog 3	
16to1MUX_TB.sv	✓	SystemVerilog 5	
16to1MUX.sv	✓	SystemVerilog 4	
4to1MUX_TB.sv	✓	SystemVerilog 2	
4to1MUX.sv	✓	SystemVerilog 0	
4bitBarrelShifter.s...	✓	SystemVerilog 1	

Digital Systems 1 – CA2
Samira Hajizadeh 810198378

E)

